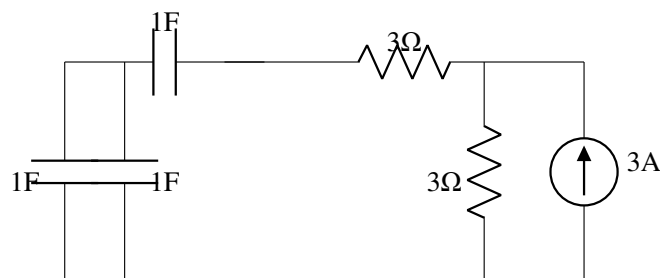



# 2008-EE-18-34

AI24BTECH11011 - Himani Gourishetty

- 1) A 3-phase Voltage source Inverter is operated in  $180^\circ$  conduction mode. Which one of the following statements is true?
  - a) Both pole-voltage and line-voltage will have  $3^{rd}$  harmonic components
  - b) Pole-voltage will have  $3^{rd}$  harmonic components but line-voltage will be free from  $3^{rd}$  harmonic
  - c) Line-voltage will have  $3^{rd}$  harmonic components but pole-voltage will be free from  $3^{rd}$  harmonic
  - d) Both pole-voltage and line-voltage will be free from  $3^{rd}$  harmonic components
- 2) The impulse response of a causal linear time-invariant system is given as  $h(t)$ . Now consider the following two statements:  
 Statement (I): Principle of superposition holds  
 Statement (II):  $h(t) = 0$  for  $t < 0$   
 Which one of the following statements is correct?
  - (A) Statement (I) is correct and Statement (II) is wrong
  - (B) Statement (II) is correct and Statement (I) is wrong
  - (C) Both Statement (I) and Statement (II) are wrong
  - (D) Both Statement (I) and Statement (II) are correct
- 3) It is desired to measure parameters of 230v/115v, 2kVA, single-phase transformer. The following wattmeters are available in a laboratory.  
 $W_1$  : 250V, 10A, Low Power Factor  
 $W_2$  : 250v, 5A, Low Power Factor  
 $W_3$  : 150V, 10A, High Power Factor  
 $W_4$  : 150V, 5A, High Power Factor  
 The wattmeters used in open circuit test and short circuit test of the transformer will respectively be
  - a)  $W_1$  and  $W_2$
  - b)  $W_2$  and  $W_4$
  - c)  $W_1$  and  $W_4$
  - d)  $W_2$  and  $W_3$
- 4) The time constant for the given circuit will be




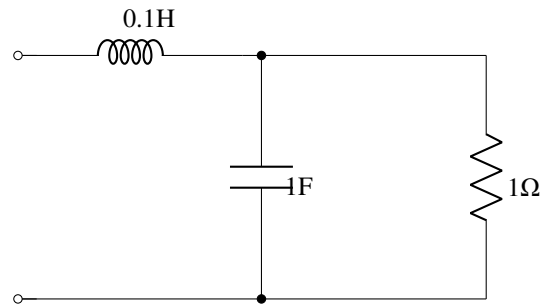- a)  $\frac{1}{9}$  s
  - b)  $\frac{1}{4}$  s
  - c) 4s
  - d) 9s
- 5) The resonant frequency for the given circuit will be



- a)  $1 \frac{rad}{s}$
- b)  $2 \frac{rad}{s}$
- c)  $3 \frac{rad}{s}$
- d)  $4 \frac{rad}{s}$

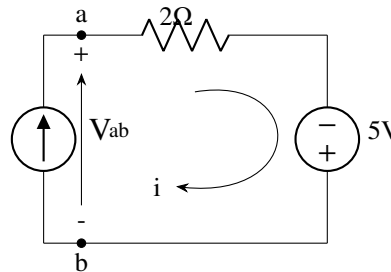6) Assuming ideal elements in a circuit shown below, the voltage  $V_{ab}$  will be



- a) -3V
- b) 0V
- c) 3V
- d) 5V

7) A capacitor consists of 2 metal plates each  $500 \times 500 \text{ mm}^2$  and spaced 6 mm apart. The space between the metal plates is filled with glass plate of 4mm thickness and a layer of paper of 2mm thickness. The relative permittivities of the glass and paper are 8 and 2 respectively. Neglecting the fringing effect, the capacitance will be (Given that  $\epsilon_0 = 8.85 \times 10^{-12} \frac{F}{m}$ )


- a) 983.33pF
- b) 1475 pF
- c) 6637.5 pF
- d) 9956.25 pF

8) A coil of 300 turns is wound on a non-magnetic core having a mean circumference of 300mm and a cross-sectional area of  $300 \text{ mm}^2$ . The inductance of the coil corresponding to a magnetizing current of 3A will be (Given that  $\mu_0 = 4\pi \times 10^{-7}$ )

- a)  $37.68 \mu H$
- b)  $113.04 \mu H$
- c) 37.68 mH
- d) 113.04 mH

9) In the circuit shown in the figure, the value of the current  $i$  will be given by

- a) 0.31A
- b) 1.25A
- c) 1.75A

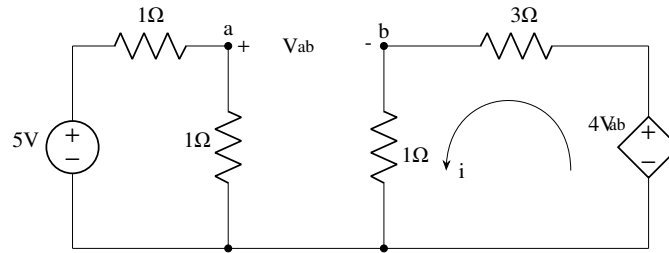

- d) 2.5A
- 10) Two point charges  $Q_1 = 10\mu C$  and  $Q_2 = 20\mu C$  are placed at coordinates  $(1, 1, 0)$  and  $(-1, -1, 0)$  respectively. The total electric flux passing through a plane  $z = 20$  will be
- $7.5\mu C$
  - $135\mu C$
  - $15.0\mu C$
  - $22.5\mu C$
- 11) Given a sequence  $x[n]$ , to generate the sequence  $y[n] = x[3 - 4n]$ , which one of the following procedures would be correct?
- First delay  $x[n]$  by 3 samples to generate  $z_1[n]$ , then pick every  $4^{th}$  sample of  $z_1[n]$  to generate  $z_2[n]$ , and then finally time reverse  $z_2[n]$  to obtain  $y[n]$
  - First advance  $x[n]$  by 3 samples to generate  $z_1[n]$ , then pick every  $4^{th}$  sample of  $z_1[n]$  to generate  $z_2[n]$ , and then finally time reverse  $z_2[n]$  to obtain  $y[n]$
  - First pick every fourth sample of  $x[n]$  to generate  $V_1[n]$ , time-reverse  $v_1[n]$  to obtain  $v_2[n]$ , and finally advance  $v_2[n]$  by 3 samples to obtain  $y[n]$
  - First pick every fourth sample of  $x[n]$  to generate  $V_1[n]$ , time-reverse  $v_1[n]$  to obtain  $v_2[n]$ , and finally delay  $v_2[n]$  by 3 samples to obtain  $y[n]$
- 12) A system with input  $x(t)$  and output  $y(t)$  is defined by the input-output relation:

$$y(t) = \int_{-\infty}^{-2t} x(\tau) d\tau \quad (1)$$

The system will be

- casual, time-invariant and unstable
  - casual, time-invariant and stable
  - non-casual, time-invariant and unstable
  - non-casual, time-invariant and unstable
- 13) A signal  $x(t) = \sin c(\alpha t)$  where  $\alpha$  is a real constant ( $\sin c(x) = \frac{\sin(\pi x)}{\pi x}$ ) is the input to a Linear Time invariant system whose impulse response  $h(t) = \sin c(\beta t)$  where  $\beta$  is a real constant. If  $\min(\alpha, \beta)$  denotes the minimum of  $\alpha$  and  $\beta$ , and similarly  $\max(\alpha, \beta)$  denotes the maximum of  $\alpha$  and  $\beta$ , and  $K$  is a constant, which one of the following statements is true about the **output of the system**?
- It will be of the form  $K \sin c(\gamma t)$  where  $\gamma = \min(\alpha, \beta)$
  - It will be of the form  $K \sin c(\gamma t)$  where  $\gamma = \max(\alpha, \beta)$
  - It will be of the form  $K \sin c(\alpha t)$
  - It cannot be a  $\sin c$  type of signal
- 14) Let  $x(t)$  be a periodic signal with time period  $T$ . let  $y(t) = x(t - t_0) + x(t + t_0)$  for some  $t_0$ . The Fourier Series coefficients of  $y(t)$  are denoted by  $b_k$ . If  $b_k = 0$  for all odd  $k$ , then  $t_0$  can be equal to
- $\frac{T}{8}$
  - $\frac{T}{4}$
  - $\frac{T}{2}$
  - $2T$

- 15)  $H(z)$  is a transfer function of a real system. When a signal  $x[n] = (1 + j)^n$  is the input to such a system, the output is zero. Further, the Region of Convergence (ROC) of  $\left(1 - \frac{1}{2}z^{-1}\right)H(z)$  is the entire Z-plane (except  $z = 0$ ). It can then be inferred that  $H(z)$  can have a minimum of
- one pole and one zero
  - one pole and two zeros
  - two poles and one zero
  - two poles and two zeros
- 16) Given  $X(z) = \frac{z}{(z-a)^2}$  with  $|z| > a$ , the residue of  $X(z)z^{n-1}$  at  $z = a$  for  $n \geq 0$  will be
- $a^{n-1}$
  - $a^n$
  - $na^n$
  - $na^{n-1}$
- 17) Consider function  $f(x) = (x^2 - 4)^2$  where  $x$  is a real number. Then the function has
- only one minimum
  - only two minima
  - three minima
  - three maxima